


PLL for Clock Synthesis Design Steps

1. Let the available crystal oscillator frequency be F_{ref}
2. Design a VCO that generates the desired frequency ($F_{desired}$) at a control voltage $V_{control} = V_{dd}/2$
3. Design divide by N counter such that $N = F_{desired} / F_{ref}$
4. Design Charge Pump PFD having charge pump current I_{CP}
5. Chose loop bandwidth of the loop filter $F_{loop} < F_{ref}/20$
6. Calculate R_s of the loop filter using the equation $F_c = \frac{R_s \times I_{cp} \times K_{vco}}{2\pi N}$
7. Chose zero frequency of the loop filter $F_z \leq F_c/3$
8. Calculate C_s of the loop filter using the equation $F_z = \frac{1}{2\pi R_s C_s}$
9. Chose pole frequency of the loop filter $F_p \geq 3F_c$
10. Calculate C_p of the loop filter using equation $F_p = \frac{1}{2\pi R_s C_p}$
11. Adjust the values of C_s and C_p (while satisfying $3.F_z < F_c < F_p/3$) so that $C_s/C_p \approx 10$. This is to ensure a phase margin of greater than 50° and stability of the PLL

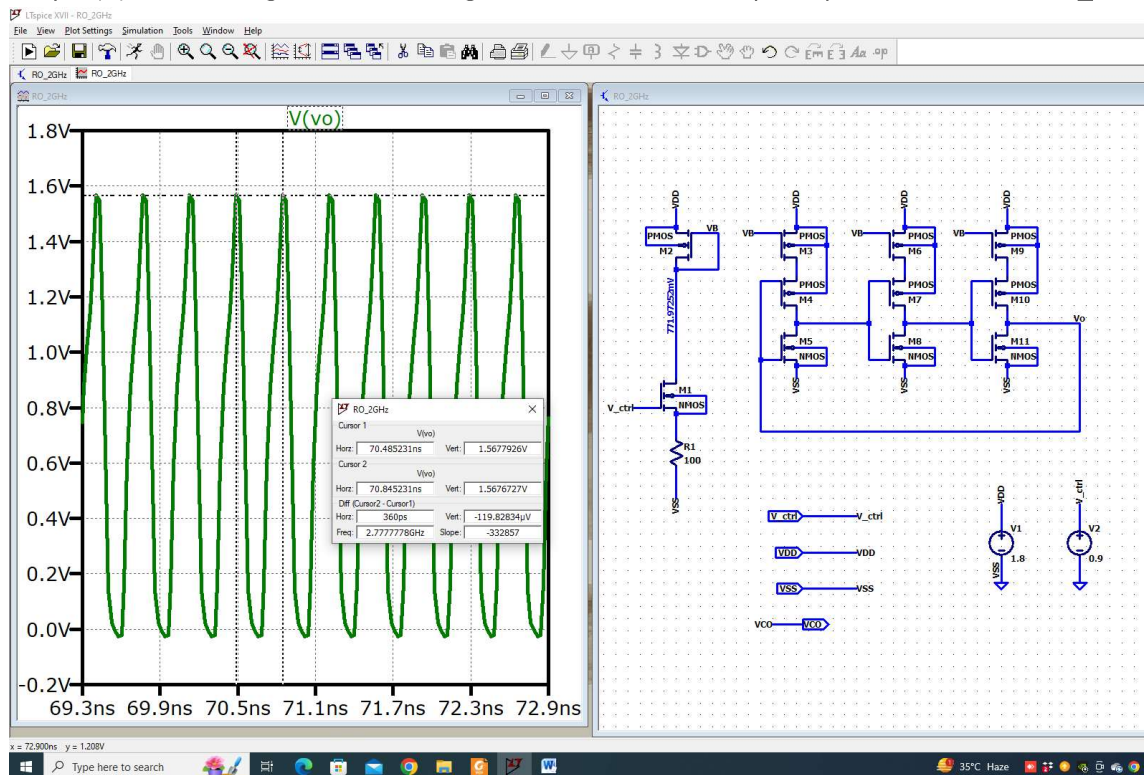
Example: Design a PLL to generate/synthesize a clock frequency of 2.5 GHz

Step-1: Let the available crystal oscillator be of $F_{ref} = 62.5$ MHz

Step-2(a): A 3 stage RO is designed to have a frequency 2.7789 GHz at $V_{control} = 0.9V$.



 Step-2(b): K_{vco} of the designed oscillator is measured to be 6.8988 GHz/V



Step-3: A divide by 40 counter is designed. Since $2.5\text{GHz} / 62.5\text{ MHz} = 40$.

Step-4: A PFD with $I_{CP} = 15\text{ uA}$ is designed using D Flip-flop, NAND gate and current mirror

Step-5: Let loop band width of loop filter be $F_C = 62.5\text{ MHz} / 25 = 2.5\text{ MHz}$

Step-6: $R_S = (2\pi N \times 2.5\text{ MHz}) / (15\text{ uA} \times 6.8988\text{ GHz/V}) = 6\text{ kOhm}$


Step-7: Let zero frequency be $F_Z = 2.5\text{ MHz} / 3 = 0.833\text{ MHz}$

Step-8: Capacitor $C_S = 1 / (2\pi \times 6\text{ k}\Omega \times 0.8333\text{ MHz}) = 31.8\text{ pF}$

Step-9: Let pole frequency $F_P = 3 \times 2.5\text{ MHz} = 7.5\text{ MHz}$


Step-10: Capacitor $C_P = 1 / (2\pi \times 6\text{ k}\Omega \times 7.5\text{ MHz}) = 21\text{ pF}$

 Step-11: With the above values of C_S and C_P , the Phase Margin = 11° only. PLL not stable. Therefore, let $C_P = 3.3\text{p pF}$ and $C_S = 33\text{ pF}$




 This DFF is connected to get a clock output with 50% duty cycle. However, the output frequency is 1.25 GHz





 2.63 GHz frequency is obtained at the input of DFF/ divider



1.259 GHz frequency is obtained at the output of the DFF